

No. of Pages	1
No. of Questions	4

Department of Computer Science and Engineering
Solution: MIDTERM EXAMINATION Spring 2019
CSE260: Digital Logic Design
Total Marks: 40 **Time Allowed: 1 Hour**

Answer ALL questions (Understanding the question is a part of the exam.)

Question No. 1

10 marks

- a) The price of $(2)_3$ pens is $(A)_{16}$ taka. (How many) $_2$ pens can Lina buy with $(23)_{10}$ takas?
 If we convert all the numbers into decimal base:
 The price of 2 pens is 10 taka. How many pens can Lina buy with 23 takas?

Price of 1 pen = $10/2 = 5$ takas

So, Lina can buy $23/5 = 4$ pens with 23 takas ;[as fractional number of pens is not possible]

So the answer is $(100)_2$

- b) How much money has she got left after buying the pens? Use a 6 bit 2s complement system to find that out.

She initially had 23 takas

She used 20 takas to buy 4 pens

So, we have to do $23-20$ in 6 bit 2s complement system

$23-20$

$= 23 + (2s \text{ com of } 20)$

$= 010111 + (2s \text{ com of } 010100)$

$= 010111 + 101100$

$= 1000011$

There is an end carry, which we have to ignore

So, the result is $= 000011$; which equals to 3 takas

Question No. 2

10 marks

$$F(x,y,z)=x'z+y+x$$

- a) Convert the above boolean equation into POS format.

$$F(x,y,z)=(x+y+z) = \prod (0)$$

- b) Draw the equivalent circuit of the given equation using only NAND gates

Question No. 3

10 marks

$$F(a,b,c,d)=a'bc+ab'c+abc'+abd+abcd+b'cd$$

Simplify the above equation using K-map and draw the simplified logic circuits using basic gates only.

$$F(a,b,c,d)=\sum(3,6,7,10,11,12,13,15)$$

Map

	$\overline{C}\overline{D}$	$\overline{C}D$	$C\overline{D}$	CD
$\overline{A}\overline{B}$	0	0	1	0
$\overline{A}B$	0	0	1	1
$A\overline{B}$	1	1	1	0
AB	0	0	1	1


Map Layout

	$\overline{C}\overline{D}$	$\overline{C}D$	$C\overline{D}$	CD
$\overline{A}\overline{B}$	0	1	3	2
$\overline{A}B$	4	5	7	6
$A\overline{B}$	12	13	15	14
AB	8	9	11	10

Groups

(3,7,11,15)	$C\overline{D}$
(6,7)	$\overline{A}B.C$
(10,11)	$A\overline{B}.C$
(12,13)	$A.B.\overline{C}$

$y = CD + A'BC + AB'C + ABC'$

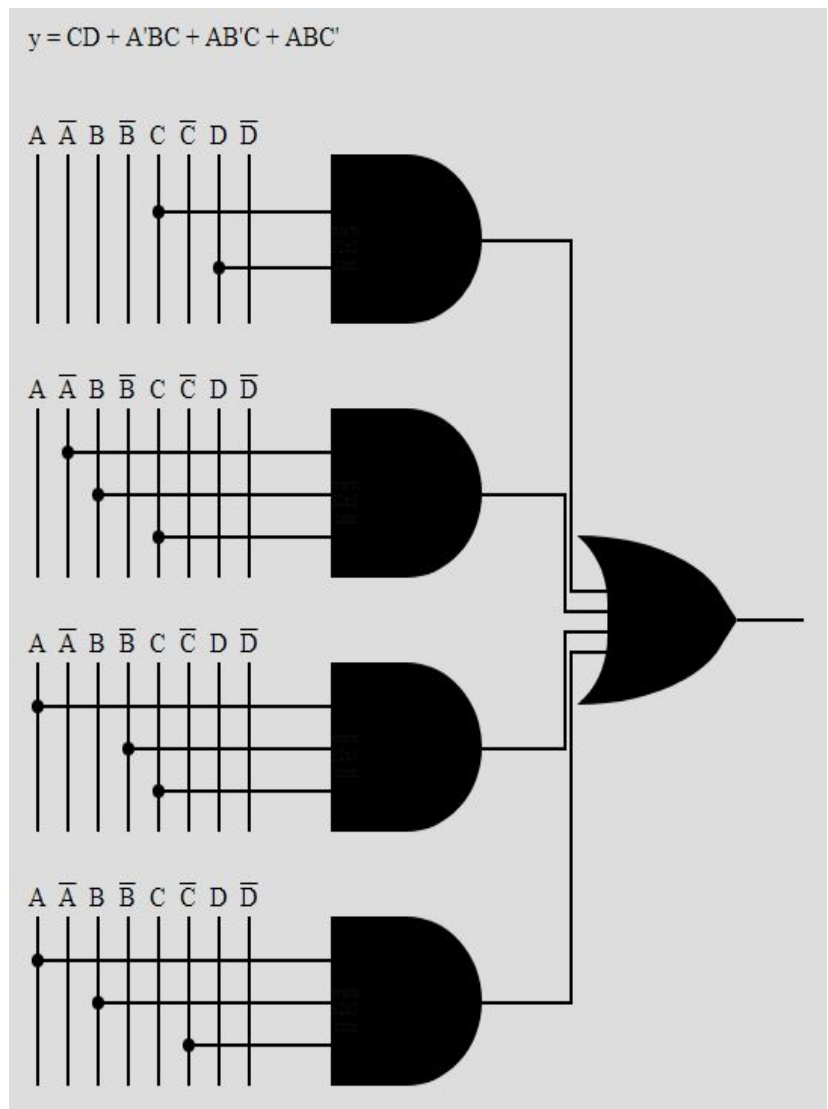

Question No. 4

10 marks

$F(A,B,C) = \sum(1,2,3,7) + d(4,5)$
Simplify the above equation using Quine-McCluskey method.

Input	First Comparasion	Second Comparasion
0	0	0
1 <div> <div>m1001</div> <div>m2010</div> <div>d4100</div> </div>	1 <div> <div>(3,1)0-1</div> <div>(5,1)-01</div> <div>(3,2)01-</div> <div>(5,4)10-</div> </div>	1 <div> <div>(7,5,3,1)-1</div> </div>
2 <div> <div>m3011</div> <div>d5101</div> </div>	2 <div> <div>(7,3)-11</div> <div>(7,5)1-1</div> </div>	
3 <div> <div>m7111</div> </div>		

Prime Implicants

(7,5,3,1)-1
(3,2)01-
(5,4)10-

Coverage Table

	-1	01-	10-
1	X		
2		X	
3	X	X	
7	X		

Essential Prime Implicants

$$A'B + C$$