

Parity Generator And Checker

Silab Zaharin

20101402

Section: 11

Name of Experiment: Parity Generator and Checker

Objective:

→ To design and implement an Even Parity checker using XOR gates (IC - 7486)


Required Components:

(i) Logic states

(ii) Wire


(iii) X-OR gate

(iv) Logic PROBE

 


Experimental Setup:


Even Parity Generator

 

Even Parity checker

 

IC

 

Generator: I have take 4 logic states, denoted as D_0, D_1, D_2, D_3 . Then $D_0 \& D_1$ is connected to a XOR gate and $D_2 \& D_3$ is connected to another XOR gate. The both of the output is connected to another XOR gate, which is Parity bit.

Even Parity Checker: Here four logic states have connected with two unique XOR gate. D_0, D_1, D_2, D_3 are those. The two output is connected to another XOR gate where P was and initial input. here we get E.

Results is Tabulated form:

From Even priority Generator

| D_3 | D_2 | D_1 | D_0 | Parity | Transmitted data |
|-------|-------|-------|-------|--------|------------------|
| 0 | 1 | 1 | 1 | 1 | 10111 |
| 0 | 1 | 0 | 1 | 0 | 01001 |
| 1 | 0 | 0 | 1 | 0 | 00000 |
| 0 | 0 | 0 | 0 | 1 | 10100 |
| 0 | 1 | 0 | 0 | | |

01111

$$D_0 \oplus D_1 = D_0' D_1 + D_1 D_0 = 0 + 0 = 0$$

$$D_2 \oplus D_3 = D_2 D_3' + D_3' D_2 = 1 + 1 = 1$$

$$\therefore Q \oplus 1 = 1$$

1001

$$D_0 \oplus D_1 = D_0' D_1 + D_1 D_0 = 0 + 1 = 1$$

$$D_2 \oplus D_3 = D_2' D_3 + D_3' D_2 = 0 + 1 = 1$$

$$\therefore 1 \oplus 1 = 0$$

0000

$$D_0 \oplus D_1 = 0 + 1 = 0$$

$$D_2 \oplus D_3 = 0 + 0 = 0$$

$$\therefore 0 \oplus 0 = 0$$

0100

$$D_0 \oplus D_1 = 0 + 1 = 1$$

$$D_2 \oplus D_3 = 0 + 0 = 0$$

$$\therefore 1 \oplus 0 = 1$$

Parity Checker:

| P | D ₃ | D ₂ | D ₁ | D ₀ | Generated Parity | Error | Output |
|---|----------------|----------------|----------------|----------------|------------------|-------|--------|
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |

Discussion: From the parity checker, we can notice that the calculation is correct because the calculation of generated parity and given parity, the error and the output from the circuit is similar.

From this experiment, we can learn about parity bit generation using logic gates and can implement.